



Teachingninja.in



Latest Govt Job updates



Private Job updates



Free Mock tests available

Visit - teachingninja.in

UPPCL AE

**Previous Year Paper
EE 1 January 2019 Shift 1**





Uttar Pradesh Power Corporation Limited

Participant ID:	
Participant Name:	
Test Center Name:	
Test Date:	01/01/2019
Test Time:	9:00 AM - 12:00 PM
Subject:	Electrical Engineering

Note

A. This is the provisional answer sheet. After considering all the complaints and suggestions, the final answer script will be released by 14 January 2019.
B. The correct answer key is mentioned with the sign (✓). Candidate's response is mentioned as the 'Chosen Option' on the right.

Section : EE (1 Mark)

Q.1 For a non-ideal single-phase transformer, which of the following is not true?

Ans A.

Short circuit test reveals approximately the resistance and leakage reactance of the transformer windings.

B.

Open circuit test is usually done on the low voltage side of a transformer.

C.

Open circuit test can reveal resistance and leakage reactance of transformer windings.

D.


Open circuit test reveals approximately the magnetizing inductance and the core-loss resistance.

Question ID : 2449922513

Status : Answered

Chosen Option :

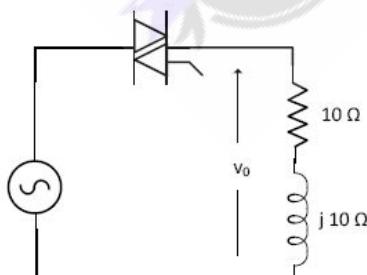Q.2 A triac based single phase voltage regulator feeds an R-L load as shown in the figure. What is the range of triggering angle for which the output voltage v_o is not controllable?



Ans A. $45^\circ \leq \alpha \leq 180^\circ$

B. $45^\circ \leq \alpha \leq 90^\circ$

C. $0^\circ \leq \alpha \leq 45^\circ$


D. $90^\circ \leq \alpha \leq 180^\circ$

Question ID : 2449922541

Status : Answered

Chosen Option :

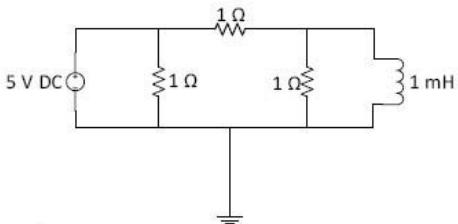Q.3 In the given circuit, with the shown ideal 5V DC source, the magnitude of the total current drawn from the source at steady-state is



Ans A. 2.5 A
 B. 5 A
 C. 10 A
 D. 7.5 A

Question ID : 2449922509

Status : Answered

Chosen Option :

Q.4 The impulse response of a causal linear time-invariant system is given as $h(t)$. Now consider the following two statements:

P: The system satisfies superposition principle.

Q: $h(t) = 0$ for $t < 0$.

Which of the following is true?

Ans A. P is false and Q is true.
 B. P is false and Q is false.
 C. P is true and Q is false.
 D. P is true and Q is true.

Question ID : 2449922508

Status : Answered

Chosen Option :

Q.5 What is the total electric flux through the surface of a sphere that has a radius of 1 m and carries a charge of $1 \mu C$ at its centre? Coulomb constant is given by $k_e = \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 N.m^2/C^2$; ϵ_0 is the permittivity of free space.

Ans A. $1.13 \times 10^5 N.m^2/C$
 B. $8.99 \times 10^3 N.m^2/C$
 C. $3.98 \times 10^3 N/C$
 D. $0.28 \times 10^5 N.m^2$

Question ID : 2449922534

Status : Not Answered

Chosen Option : --

Q.6

A DC-DC buck-boost converter is operated with continuous current mode. If the input voltage is 50 V and the duty cycle of the switch is 0.6, the output DC voltage is

Ans A. 35 V
 B. 75 V
 C. 65 V
 D. 50 V

Question ID : 2449922540

Status : Answered

Chosen Option :

Q.7 The minimum phase attained for the frequency response of a causal system $G(s) = \frac{s+10}{(s+1)(s+2)}$ as the frequency varies from 0 to ∞ rad/s is


Ans A. 180 degrees
 B. 90 degrees
 C. -90 degrees
 D. -180 degrees

Question ID : 2449922505

Status : Answered

Chosen Option :

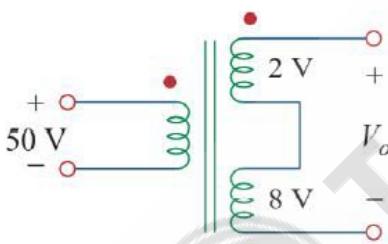Q.8 A three-winding transformer is connected to an AC source with 50 V rms as shown in the following figure. Voltages induced in the secondary windings are 2 V rms and 8 V rms. The output rms voltage V_o is,



Ans A. -6 V
 B. 10 V
 C. -10 V
 D. 6 V


Question ID : 2449922530

Status : Answered

Chosen Option :

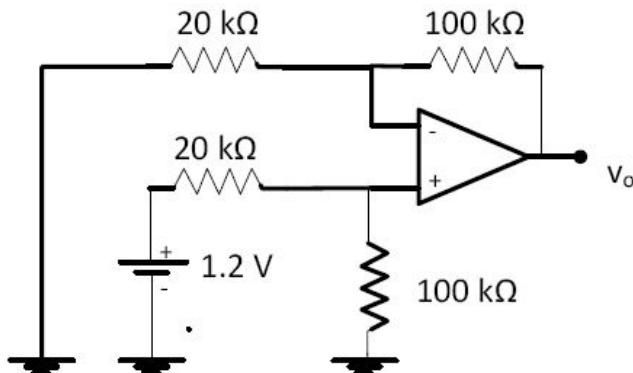Q.9

The op-amp in the circuit shown in the figure works in linear mode. The output voltage v_o is



Ans

- A. 5 V
- B. 6 V
- C. 1 V
- D. 4 V

Question ID : 2449922543

Status : Answered

Chosen Option :

Q.1 For operation in the normal active mode for a BJT, which of the following conditions is true?

0

Ans

- A. Both B-E and C-B junctions should be reversed biased.
- B. Both B-E and C-B junctions should be forward biased.
- C. B-E junction should be reversed biased and C-B junction should be forward biased.
- D. B-E junction should be forward biased and C-B junction should be reversed biased.

Question ID : 2449922544

Status : Answered

Chosen Option :

Q.1 A single phase full bridge voltage source inverter is operated with SPWM (sinusoidal pulse width modulation). The input DC voltage is 100 V. If the amplitude modulation index is 1, the rms value of fundamental component of output voltage is

1

Ans

- A. 141.4 V
- B. 70.7 V
- C. 50.3 V
- D. 90.7 V


Question ID : 2449922539

Status : Answered

Chosen Option :

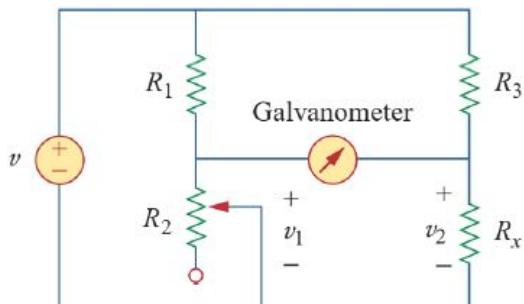Q.1
2

In the given Wheatstone bridge, $R_1 = 500 \Omega$, $R_3 = 200 \Omega$. The bridge is balanced when R_2 is adjusted to 125Ω . Determine the unknown resistance R_x .



Ans A. $R_x = 100 \Omega$
 B. $R_x = 200 \Omega$
 C. $R_x = 50 \Omega$
 D. $R_x = 125 \Omega$

Question ID : 2449922529

Status : Answered

Chosen Option :

Q.1
 3 The causal system represented by $G(s) = \frac{9}{s^2+6s+9}$ is

Ans A. Undamped
 B. Underdamped
 C. Critically damped
 D. Overdamped

Question ID : 2449922504

Status : Answered

Chosen Option :

Q.1
 4 The average output voltage of a half controlled bridge converter is measured to be 103.53 V. If the bridge is supplied from a 230 V, 50 Hz sinusoidal source, the triggering angle of the thyristors in the bridge is approximately

Ans A. 60°
 B. 90°
 C. 120°
 D. 30°

Question ID : 2449922537

Status : Answered

Chosen Option :

Q.1
 5 Auto-transformer is used in the transmission and distribution systems

Ans A. When galvanic isolation is needed.
 B. When operator is not available
 C. When efficiency of transformer is not critical

D. When the transformation ratio for voltage is small

Question ID : 2449922523

Status : Answered

Chosen Option :

Q.1 The compensating winding in a DC machine
6


Ans A. is located on the commutating poles.
 B. is located on commutators.
 C. is located in armature slots.
 D. is located on pole shoes.

Question ID : 2449922512

Status : Answered

Chosen Option :

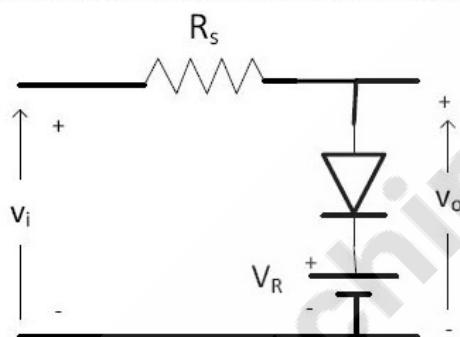Q.1 In the diode circuit shown in the figure, $v_i = 10\sin 314.159t$ V and $V_R = 5$ V. Assume the diode
7 to be ideal. The maximum and minimum values of the output voltage (v_o) are, respectively,



Ans A. +10 V and -5 V
 B. +5 V and -10 V
 C. +5 V and -5 V
 D. 10 V and -10 V

Question ID : 2449922547

Status : Answered

Chosen Option :

Q.1 A load-flow program is run twice. In the second run, the previous reference bus gets changed to
8 a PQ bus. Which one of the following statements is true?

Ans A. The system losses as well as complex bus voltages will change.
 B. Load flow result will remain same in all aspects.
 C.

The system losses will change but the complex bus voltages will remain same.

D.

The system losses will be unchanged but the complex bus voltages will change.

Question ID : 2449922519

Status : Answered

Chosen Option :

Q.1 In a balanced *acb* sequence, phase *a* to neutral voltage is $\bar{V}_{an} = 100\angle 20^\circ$ V. Line-to-line voltage
9 \bar{V}_{ac} is given by

Ans A. $\bar{V}_{ac} = 100\sqrt{3}\angle 50^\circ$ V
 B. $\bar{V}_{ac} = 100\sqrt{3}\angle -50^\circ$ V
 C. $\bar{V}_{ac} = 100\angle 50^\circ$ V
 D. $\bar{V}_{ac} = \frac{100}{\sqrt{3}}\angle 150^\circ$ V

Question ID : 2449922532

Status : Answered

Chosen Option :

Q.2 A 3-phase transformer bank is realized using three identical 1100/230 V, 10 kVA single phase
0 transformers connected in delta-delta. If one of the single phase transformers develops a fault
and is removed, the maximum load that the transformer bank in open delta can supply is

Ans A. 5.77 kVA
 B. 11.54 kVA
 C. 17.32 kVA
 D. 30 kVA

Question ID : 2449922550

Status : Answered

Chosen Option :

Q.2 The purpose of emitter bypass capacitor in a CE BJT amplifier is to
1

Ans A. prevent saturation of the amplifier
 B. place the Q-point of the transistor in active region
 C. provide a stable biasing for the amplifier
 D. increase the mid band voltage gain of the amplifier

Question ID : 2449922546

Status : Answered

Chosen Option :

Q.2 A Buchholz relay is used for
2

Ans A. Protection of a transformer against internal and external faults
 B. Protection of a transformer against internal faults
 C. None of the options
 D. Protection of a transformer against external faults


Question ID : 2449922520

Status : Answered

Chosen Option :

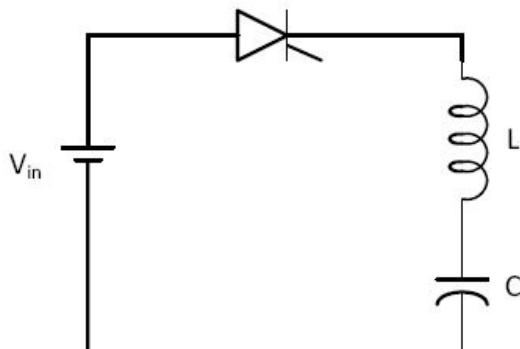Q.2
3

The SCR in the circuit is turned on at $t = 0$. The conduction time duration of the SCR is



Ans A. $2\pi\sqrt{LC}$
 B. $\pi\sqrt{LC}$
 C. \sqrt{LC}
 D. $1/(2\pi\sqrt{LC})$

Question ID : 2449922542

Status : Answered

Chosen Option :

Q.2 4 A sequence $u[n]$ is defined as $u[n] = \begin{cases} 1, & \text{if } n \geq 0 \\ 0, & \text{if } n < 0 \end{cases}$ for $n = \{-\infty, \dots, -1, 0, 1, \dots, \infty\}$. The z-transform of $u[n]$ is $U(z)$. The region of convergence for which the z-transform of $u[n]$ exists is

Ans A. $|z| > 1$
 B. $|z| < 1$
 C. $|z| = 1$
 D. $|z| > 0$

Question ID : 2449922511

Status : Answered

Chosen Option :

Q.2 5 The graph of an electrical network has N nodes and B branches. The number of links, L , for any tree spanning all nodes is given by

Ans A. $B+N$
 B. $N-B+1$
 C. $N-2B+1$
 D. $B-N+1$

Question ID : 2449922525

Status : Answered

Chosen Option :

Q.2 6 A single phase power transformer is to be energized (switched on to the input supply) to have minimal inrush current. The switching-on instant should be at

Ans A. Zero input voltage
 B. $\frac{1}{2}$ of the maximum input voltage
 C. Maximum input voltage

D. $1/\sqrt{2}$ of the maximum input voltage

Question ID : 2449922549

Status : Answered

Chosen Option :

Q.2 Consider the following Laplace transforms of certain signals. For which of the following, final value theorem is not applicable?

Ans

A. $\frac{s-1}{s+2}$

B. $\frac{s+1}{s+2}$

C. $\frac{s+1}{(s+2)(s+3)}$

D. $\frac{s+1}{s-2}$

Question ID : 2449922502

Status : Answered

Chosen Option :

Q.2 Consider a signal $g(t)$, such that $g(t) = 0$ for $t < 0$. If the Laplace transform of $g(t)$ is $G(s)$, then with constant τ , the Laplace transform of $g(t - \tau)$ is

Ans

A. $G(s + \tau)$

B. $e^{s\tau} G(s\tau)$

C. $e^{-s\tau} G(s)$

D. $G(s - \tau)$

Question ID : 2449922507

Status : Answered

Chosen Option :

Q.2 Two inductors of 5 H and 4 H have mutual inductance of 2.5 H between them. The coupling coefficient is

Ans

A. 1.78

B. 0.125

C. 0.56

D. 4.47

Question ID : 2449922533

Status : Answered

Chosen Option :

Q.3 To ensure successful turn-on of a thyristor, the minimum gate pulse width of the thyristor gate pulse should be sufficient to ensure the cathode current to reach

Ans

A. the holding value of thyristor current

B. the peak value of thyristor current

C. the latching value of thyristor current
 D. 50% of the peak value of thyristor current

Question ID : 2449922538

Status : Answered

Chosen Option :

Q.3 1 The transfer function $G(s) = \frac{1}{s^2}$ has a 0 dB crossing in its Bode magnitude plot at


Ans A. 100 rad/s.
 B. 10 rad/s.
 C. 0.1 rad/s.
 D. 1 rad/s.

Question ID : 2449922501

Status : Answered

Chosen Option :

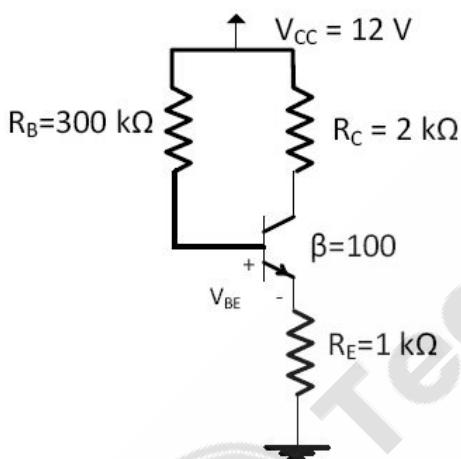Q.3 2 A BJT biasing circuit is shown in the figure. The transistor is operating in the active region with $V_{BE} = 0.7$ V. The value of collector current in mA is



Ans A. 4.813
 B. 1.210
 C. 3.512
 D. 2.817

Question ID : 2449922545

Status : Answered

Chosen Option :

Q.3 3 Inductance of a power transmission line increases with

Ans A. Increase in diameter of the conductor
 B. Decrease in line length
 C. Increase in spacing between the phase conductors
 D. Increase in load current carried by the conductor

Question ID : 2449922521

Status : **Answered**
Chosen Option :

Q.3 The following are various energy sources:
4

1. Solar
2. Wind
3. Tidal
4. Wave
5. Geo-thermal

From the above energy sources, the renewable energy sources are

Ans A. 1 and 2 only
 B. All the energy sources mentioned above
 C. 1, 2, and 4 only
 D. 1, 2, and 3 only

Question ID : **2449922524**
Status : **Answered**
Chosen Option :

Q.3 An ideal air-core coil has an inductance of 2 mH. The number of turns of the coil is doubled and
5 its length is halved. Assuming that the inner cross-sectional area of the core remains constant,
the new inductance of this altered air-core coil is

Ans A. 8 mH
 B. 16 mH
 C. 4 mH
 D. 32 mH

Question ID : **2449922510**
Status : **Answered**
Chosen Option :

Q.3 An electrostatic field is given by $\vec{E} = \left(\frac{x}{2} + 2y\right)\mathbf{i} + 2x\mathbf{j} \text{ V/m}$. Find the work done in moving a
6 point charge $Q = -20 \mu\text{C}$ from the origin to (4,0,0) m. (\mathbf{i}, \mathbf{j}) are the unit vectors along x, y
axes.

Ans A. $80 \mu\text{J}$
 B. $40 \mu\text{J}$
 C. 40 kJ
 D. 80 J

Question ID : **2449922536**
Status : **Answered**
Chosen Option :

Q.3 The effective charge flowing through a wire is given by, $q = 5t \sin 4\pi t \text{ mC}$. Calculate the
7 instantaneous current flowing at time $t = 0.5 \text{ s}$.

Ans A. 31.4 mA
 B. 0 A
 C. 2.5 mA

D. 3.14 A

Question ID : 2449922527

Status : Answered

Chosen Option :

Q.3 A circuit with a resistor, inductor, and capacitor in series has a resonant frequency of f_0 Hz. If all
8 the component values are now doubled, the new resonant frequency is

Ans A. $2f_0$
 B. $f_0/2$
 C. $f_0/4$
 D. f_0

Question ID : 2449922516

Status : Answered

Chosen Option :

Q.3
9 The inductance of a certain moving-iron ammeter is expressed as $L = 10 + 3\theta - \frac{\theta^2}{4} \mu\text{H}$, where θ is the deflection in radians from the zero position. The control spring torque is 25×10^{-6} Nm/radian. The deflection of the pointer in radians, when the meter carries current of 5 A rms, is


Ans A. 2.4
 B. 2.0
 C. 1.2
 D. 1.0

Question ID : 2449922515

Status : Answered

Chosen Option :

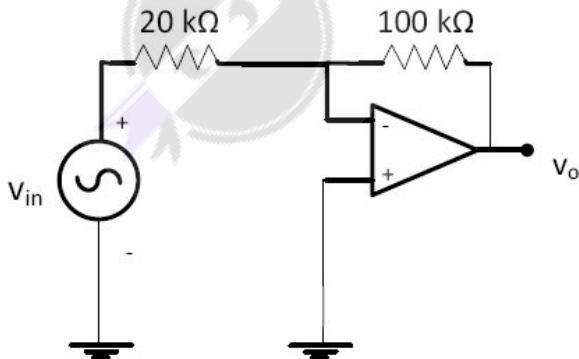Q.4 The open-loop gain-bandwidth product of an op-amp is given as 10,000 Hz. The op-amp is used
0 in an inverting amplifier as shown in the figure. The bandwidth of the inverting amplifier is



Ans A. 2000 Hz
 B. 1000 Hz
 C. 10,000 Hz
 D. 5000 Hz

Question ID : 2449922548

Status : **Answered**

Chosen Option :

Q.4 A water boiler at a home in Lucknow is switched to the AC mains supply power. The frequency of

1 instantaneous power consumed by the boiler is

Ans A. 0 Hz
 B. 50 Hz
 C. 100 Hz
 D. 150 Hz

Question ID : **2449922518**

Status : **Answered**

Chosen Option :

Q.4 A transmission line of surge impedance 300Ω is connected to a load of 300Ω . The reflection

2 coefficient of transmission line at the load end will be

Ans A. 0
 B. -1
 C. 2
 D. +1

Question ID : **2449922522**

Status : **Answered**

Chosen Option :

Q.4 A parallel-plate capacitor has an area $A = 2 \times 10^{-4} \text{ m}^2$ and a plate separation $d = 1 \text{ mm}$.

3 Permittivity of free space, $\epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2}$. Its capacitance is,


Ans A. 1.77 nF
 B. $4.23 \mu\text{F}$
 C. 4.23 nF
 D. 1.77 pF

Question ID : **2449922535**

Status : **Answered**

Chosen Option :

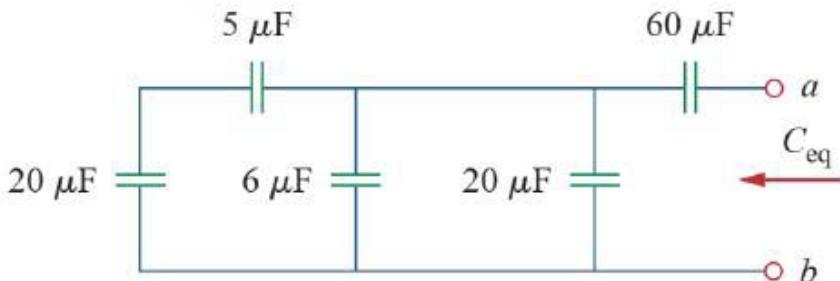Q.4 Find the equivalent capacitance, C_{eq} , at the terminals $a-b$ of the circuit.



Ans A. 20 μF
 B. 85 μF

C. $80 \mu\text{F}$
 D. $46 \mu\text{F}$

Question ID : 2449922531

Status : Answered

Chosen Option :

Q.4 ₅ Kelvin double bridge is best suited for the measurement of

Ans A. Low resistance
 B. Capacitance
 C. Inductance
 D. High resistance

Question ID : 2449922517

Status : Answered

Chosen Option :

Q.4 ₆ The time constant of the causal system represented by $G(s) = \frac{1}{s+5}$ is

Ans A. $10/\pi$ seconds
 B. 5 seconds
 C. 0.2 seconds
 D. $\pi/10$ seconds

Question ID : 2449922503

Status : Answered

Chosen Option :

Q.4 ₇ The equation $e_f = -\frac{d\phi}{dt}$, where e_f is the emf and ϕ is the flux linkage in a single-turn coil, can best represent

Ans A. Faraday's Law
 B. Faraday's Law and Lenz Law
 C. Lenz Law and Biot-Savart Law
 D. Biot-Savart Law

Question ID : 2449922526

Status : Answered

Chosen Option :

Q.4 A linear time-invariant system, initially at rest, when subjected to a unit-step input at $t = 0$, gives

₈ a response $y(t) = te^{-t}$ for $t \geq 0$. The transfer function of the system is

Ans A. $\frac{1}{s^2}$
 B. $\frac{1}{(s+1)^2}$

✓ C. $\frac{s}{(s+1)^2}$


✗ D. $\frac{1}{s(s+1)^2}$

Question ID : 2449922506

Status : Answered

Chosen Option :

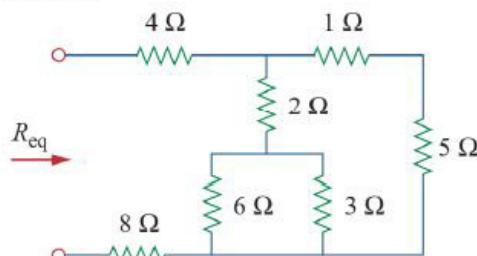Q.4 Find the equivalent resistance, R_{eq} , looking into the terminals of the following circuit as indicated.



Ans ✓ A. 14.4 Ω
✗ B. 12.4 Ω
✗ C. 15.2 Ω
✗ D. 10 Ω

Question ID : 2449922528

Status : Answered

Chosen Option :

Q.5 For an ideal single-phase transformer with primary-to-secondary turns ratio of $N:1$, the ratio of instantaneous input power to instantaneous output power is

Ans ✓ A. 1:1
✗ B. $N:1$
✗ C. $1:N$
✗ D. $N^2:1$

Question ID : 2449922514

Status : Answered

Chosen Option :

Section : EE (2 Mark)

Q.1 A sequence $u[n]$ is defined as $u[n] = \begin{cases} 1, & \text{if } n \geq 0 \\ 0, & \text{if } n < 0 \end{cases}$ for $n = \{-\infty, \dots, -1, 0, 1, \dots, \infty\}$. Consider a sequence $x[n] = n^2 a^n u[n]$, where a is a positive constant. The z-transform of the sequence with appropriate region of convergence is

Ans ✓ A. $\frac{az(z+a)}{(z-a)^3}$
✗ B. $\frac{z}{(z-a)^2}$

C. $\frac{az}{(z-a)^2}$


D. $\frac{ze^{-a}}{(z-e^{-a})^2}$

Question ID : 2449922553

Status : Answered

Chosen Option :

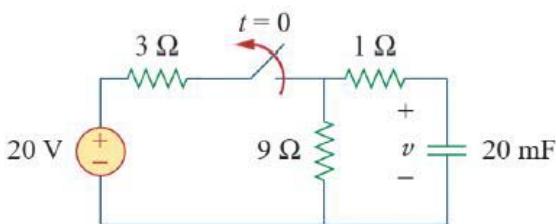Q.2 The switch in the circuit has been closed for a long time, and it is opened at time $t = 0$. Find $v(t)$ for $t \geq 0$.



Ans A. $v(t) = 15e^{-5t} \text{ V}$

B. $v(t) = 15 \text{ V}$

C. $v(t) = 0 \text{ V}$


D. $v(t) = 15e^{-20t} \text{ V}$

Question ID : 2449922567

Status : Answered

Chosen Option :

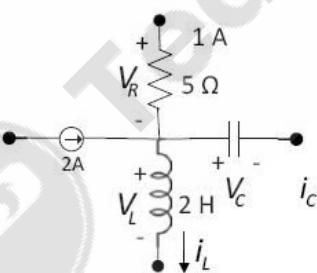Q.3 A segment of a circuit is shown in the figure below. If $V_R = 5 \text{ V}$ and $V_C = 4\sin 2t \text{ V}$, the voltage V_L is



Ans A. $32\sin 2t \text{ V}$

B. $16\cos 2t \text{ V}$

C. $3 - 8\cos 2t \text{ V}$

D. $16\sin 2t \text{ V}$


Question ID : 2449922563

Status : Answered

Chosen Option :

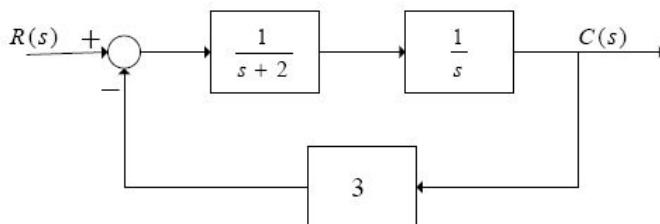Q.4

Consider the system in the figure shown. The input to the system is $R(s)$ and the output of the system is $C(s)$. The system is of Type



Ans A. 1
 B. 3
 C. 0
 D. 2

Question ID : 2449922552

Status : Answered

Chosen Option :

Q.5 The positive value of K for which $\left[1 + \frac{K}{(s+1)(s+2)}\right]$ will have zeroes on the right-half of the complex s -plane is

Ans A. 20
 B. No such K exists
 C. 0.1
 D. 10

Question ID : 2449922551

Status : Answered

Chosen Option :

Q.6 A combinatorial circuit is described by a function as the sum of min-terms. The function is defined as $f(A,B,C) = \sum m(0,1,2,3,4,5,6)$

A is the MSB and C is the LSB. The minimized expression of the function is

Ans A. ABC
 B. $\bar{B} + \bar{C}$
 C. $\bar{A} + \bar{B} + C$
 D. $\bar{A} + \bar{B} + \bar{C}$

Question ID : 2449922574

Status : Answered

Chosen Option :

Q.7 A current of $-8 + 6\sqrt{2}(\sin \omega t + 30^\circ)$ A is passed through three meters. These are a zero-centered PMMC meter, a true RMS meter, and a moving iron instrument. The respective readings (in A) will be

Ans A. 8, 6, 10
 B. -8, 6, 10
 C. 8, 6, 8


✓ D. -8, 10, 10

Question ID : 2449922562

Status : Answered

Chosen Option :

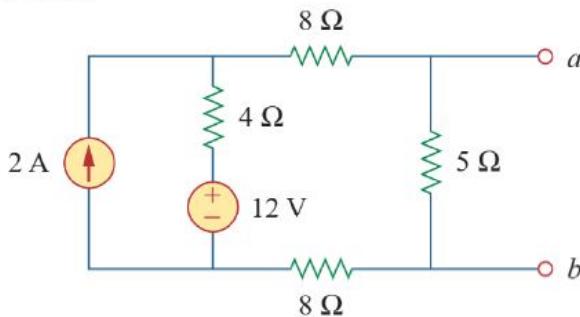Q.8 Find Norton equivalent resistance, R_N , and equivalent current source, i_N , at terminals a and b of the circuit.



Ans A. $R_N = 3.53 \Omega, i_N = 0.71 A$
 B. $R_N = 4 \Omega, i_N = 1 A$
 C. $R_N = 12 \Omega, i_N = 2 A$
 D. $R_N = 5 \Omega, i_N = 2 A$

Question ID : 2449922565

Status : Answered

Chosen Option :

Q.9 A 240 V DC shunt motor has an armature resistance of 0.6Ω . The full load armature current is 30 A. The ratio of the stalling torque to the full load torque when a resistance of 1Ω is connected in series with the armature is

Ans A. 3
 B. 6
 C. 5
 D. 4

Question ID : 2449922575

Status : Answered

Chosen Option :

Q.1
$$\int_{-\pi}^{\pi} \sin(t) \sin(3t) dt =$$

Ans A. 2π
 B. 0
 C. $\pi/2$
 D. π

Question ID : 2449922554

Status : Answered

Chosen Option :

Q.1 An ammeter with range of 0 to $100 \mu\text{A}$ has an internal resistance of 100Ω . For extending its range to 0 to $500 \mu\text{A}$, the shunt resistance required is


Ans A. 20Ω
 B. 22.22Ω
 C. 50Ω
 D. 25Ω

Question ID : 2449922561

Status : Answered

Chosen Option :

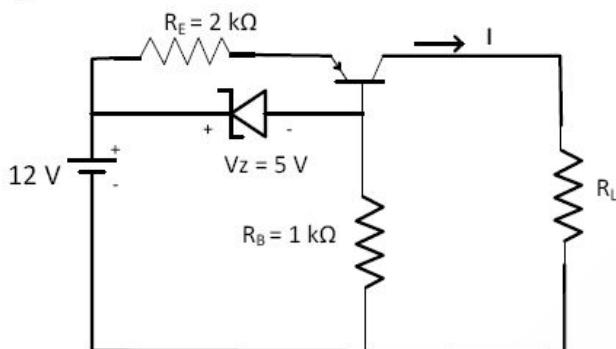Q.1 A BJT current source is given in the figure. Assume the Si-PNP transistor to operate in active region. The value of current I in mA is



Ans A. 1.85
 B. 2.15
 C. 5.25
 D. 4.1


Question ID : 2449922573

Status : Not Answered

Chosen Option : --

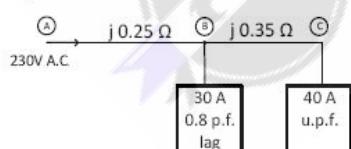Q.1 A single phase AC distribution line supplies two single phase loads as shown in the figure below.

3 The impedances of line segments A-B and B-C are $j0.25 \Omega$ and $j0.35 \Omega$, respectively. The voltage drop from A to C is



Ans A. $30 + j 4.5 \text{ V}$
 B. $4.5 + j 30 \text{ V}$
 C. $30 - j 4.5 \text{ V}$
 D. $4.5 - j 30 \text{ V}$

Question ID : 2449922559

Status : Answered

Chosen Option :

A factory draws 100 kW at 0.8 p.f. lagging from a 3-phase, 11 kV supply. It is desired to raise the p.f. to unity using capacitor bank. The total power rating of the capacitor bank is

Ans A. 75 kVAR
 B. 100 kVAR
 C. 62.5 kVAR
 D. 50 kVAR

Question ID : 2449922558

Status : Answered

Chosen Option :

Q.1 An open circuit test is conducted on a 1100/110 V, 50 Hz single-phase transformer with 5 instruments connected on the low voltage side of the transformer. The voltmeter reads 110 V. The ammeter reads 2 A. The wattmeter reading is 65 W. The approximate core-loss resistance and magnetizing reactance, referred to the low voltage side, are respectively,


Ans A. 1.8615 Ω , 0.5757 Ω
 B. 18.615 Ω , 5.757 Ω
 C. 18615 Ω , 5757 Ω
 D. 186.15 Ω , 57.57 Ω

Question ID : 2449922556

Status : Answered

Chosen Option :

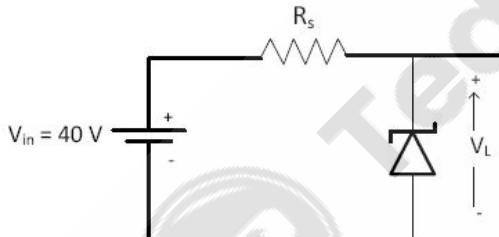Q.1 The Zener diode in the circuit has a Zener voltage, V_z , of 15 V and power rating of 0.5 Watt. If the 6 input voltage is 40 V, what is the minimum value of R_s that prevents the Zener diode from being destroyed?




Ans A. 150 Ω
 B. 250 Ω
 C. 750 Ω
 D. 550 Ω

Question ID : 2449922572

Status : Answered

Chosen Option :

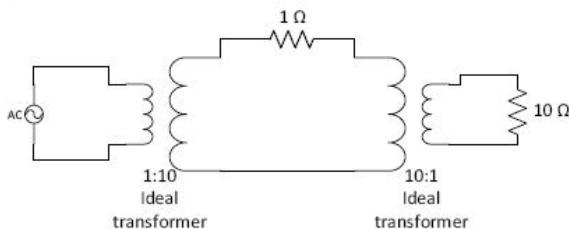In the circuit shown, assume that the voltage source and transformers are ideal. The AC voltage source is $10\sqrt{2} \sin(100\pi t)$ V. The rms value of the current flowing through the $1\ \Omega$ resistor is approximately (rounded off till first decimal place)




Ans A. 0.1A
 B. 9.1A
 C. 10.0A
 D. 0.9A

Question ID : 2449922555

Status : Answered

Chosen Option :

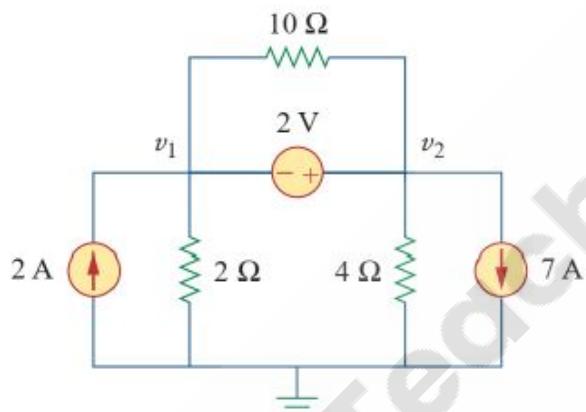Q.1 For the circuit shown in the figure, find the node voltages v_1 and v_2 .
 8




Ans A. $v_1 = 8.33\text{ V}$, $v_2 = 10.33\text{ V}$
 B. $v_1 = 6\text{ V}$, $v_2 = 8\text{ V}$
 C. $v_1 = 4\text{ V}$, $v_2 = -28\text{ V}$
 D. $v_1 = -7.33\text{ V}$, $v_2 = -5.33\text{ V}$

Question ID : 2449922564

Status : Answered

Chosen Option :

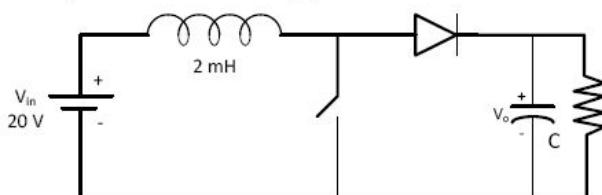Q.1 In a boost converter shown in the figure, the duty cycle is 0.5. The inductor current is assumed to
 9 be continuous. Capacitor C is assumed to be very large. If the switching frequency is 20 kHz, the peak to peak inductor current ripple is




Ans A. 0.45 A

B. 0.35 A
 C. 0.25 A
 D. 0.15 A

Question ID : 2449922571
 Status : Not Answered
 Chosen Option : --

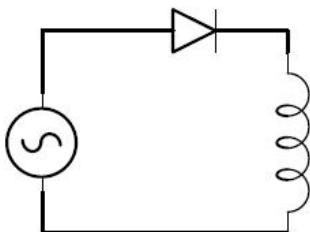Q.2 A sinusoidal AC voltage source feeds a pure inductor through a diode as shown in the figure. The duration of conduction (in degrees) of the diode in one input power cycle is



Ans A. 30°
 B. 90°
 C. 360°
 D. 180°

Question ID : 2449922570
 Status : Answered
 Chosen Option :

Q.2 A single phase full bridge voltage source inverter is operated in 180° mode with square wave output. If the input DC supply is 100 V, the rms value of the fundamental output voltage is

Ans A. 80 V
 B. 50 V
 C. 90 V
 D. 70 V

Question ID : 2449922569
 Status : Answered
 Chosen Option :

Q.2 A charge $q_1 = 7 \mu C$ is located at the origin, and a second charge $q_2 = -5 \mu C$ is located on the positive x-axis, 0.3 m from the origin. Find the electric field at point P, which has coordinates (0, 0.4) m. Coulomb constant is given by, $k_e = \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 N \cdot m^2/C^2$; ϵ_0 is the permittivity of free space; (\hat{i} , \hat{j}) are the unit vectors along x, y axes.

Ans A. $-(1.1\hat{i} + 2.5\hat{j}) \times 10^5 N/C$
 B. $(1.1\hat{i} + 2.5\hat{j}) \times 10^5 N/C$
 C. $(2.5\hat{i} - 1.1\hat{j}) \times 10^5 N/C$
 D. $-(2.5\hat{i} + 1.1\hat{j}) \times 10^5 N/C$

Question ID : 2449922568
 Status : Not Answered

Chosen Option : --

Q.2 The terminal voltage of an ideal DC voltage source is 12 V, when connected to a 2 W resistive load. When the load is disconnected, the terminal voltage rises to 12.4 V. What are the values of source voltage, v_s , and internal resistance, R_s , of the source?

Ans A. $v_s = 12 \text{ V}, R_s = 4 \Omega$
 B. $v_s = 10 \text{ V}, R_s = 8 \Omega$
 C. $v_s = 12.4 \text{ V}, R_s = 4 \Omega$
 D. $v_s = 12.4 \text{ V}, R_s = 2.4 \Omega$

Question ID : 2449922566

Status : Answered

Chosen Option :

Q.2 Incremental fuel costs in Rs/MWh for a plant consisting of two generating units are given by

$$\frac{dF_1}{dP_1} = 0.4P_1 + 400 \quad \text{and} \quad \frac{dF_2}{dP_2} = 0.48P_2 + 320$$

The allocation of loads P_1 and P_2 between generating units 1 and 2, respectively, for minimum cost of generation to serve a total load of 900 MW, neglecting losses, is

Ans A. 200 MW and 700 MW
 B. 500 MW and 400 MW
 C. 300 MW and 600 MW
 D. 400 MW and 500 MW

Question ID : 2449922557

Status : Answered

Chosen Option :

Q.2 A power system has three synchronous generators. The turbine-governor characteristics corresponding to the generators are

$$P_1 = 50(50 - f), \quad P_2 = 100(51 - f), \quad P_3 = 150(52 - f)$$

where, f denotes the system frequency in Hz, and P_1, P_2, P_3 are the power outputs of the turbines in MW. Assuming generators and transmission network to be lossless, the system frequency for a load of 700 MW is

Ans A. 49 Hz
 B. 47.5 Hz
 C. 48 Hz
 D. 49.5 Hz

Question ID : 2449922560

Status : Answered

Chosen Option :

Section : Hindi

Q.1 दिए गए विकल्पों में से कौन सा वाक्यांश नीचे लिखे शब्द का सही अर्थ है?

शब्द-: अजातशत्रु

Ans

- A. जिसके बहुत से शत्रु हों
- B. जिसका कोई भी शत्रु न हो
- C. जिससे जन्म से शत्रुता हो
- D. जन्म से शत्रुता का बोध होना

Question ID : 2449922579

Status : Answered

Chosen Option :

Q.2 दिए गए विकल्पों में से कौन सा विकल्प दिए हुए शब्द का पर्यायवाची नहीं हैं?

शब्द-: आँख

Ans

- A. चारू
- B. नयन
- C. चक्षु
- D. लोचन

Question ID : 2449922578

Status : Answered

Chosen Option :

Q.3 मुंशी प्रेमचंद की कहानी “इदगाह” में हामिद अपनी दादी के लिए मेले से क्या खरीदकर लाता हैं?

Ans

- A. चिमटा
- B. थाली
- C. बेलन
- D. तवा

Question ID : 2449922576

Status : Answered

Chosen Option :

Q.4 दिए गए विकल्पों में से कौन सा विकल्प नीचे लिखे शब्द का सही सन्धि-विग्रह है?

शब्द-: नीरस

Ans

- A. नइ + रस
- B. निः + रस
- C. नीर + रस
- D. निइ + रस

Question ID : 2449922580

Status : Answered

Chosen Option :

Q.5 दिए गए वाक्यांशों में से सर्वोचित वाक्यांश चुनकर नीचे दिए गए मुहावरे को पूरा करें।

मुहावरा:- बाल की _____

Ans

- A. कटाई करना
- B. रंगाई करना

C. खाल निकालना
 D. जड़ निकालना

Question ID : 2449922577

Status : Answered

Chosen Option :

Section : GK

Q.1 न्युरेम्बर्ग निम्नलिखित में से किस घटना से जुड़ा है?

Ans A.

द्वितीय विश्वयुद्ध की समाप्ति के बाद विश्व शांति एवं सौहार्द की चर्चा के लिए विश्व भर के नेता यहाँ एकत्र हुए थे।

B.

प्रथम विश्वयुद्ध की समाप्ति के बाद विश्व शांति एवं सौहार्द की चर्चा के लिए विश्व भर के नेता यहाँ एकत्र हुए थे।

C.

द्वितीय विश्वयुद्ध की समाप्ति के बाद यहाँ पर युद्ध अपराधियों पर मुकदमे चलाये गये थे।

D.

प्रथम विश्वयुद्ध की समाप्ति के बाद यहाँ पर युद्ध अपराधियों पर मुकदमे चलाये गये थे।

Question ID : 2449922584

Status : Answered

Chosen Option :

Q.2 'वॉर एंड पीश' (War and Peace) नामक उपन्यास के लेखक कौन हैं?

Ans A. फ्र्योदोर दोस्तोयेव्स्की

B. लियो टॉल्स्टॉय

C. अलेक्जेंडर पुज्जिन

D. मिखाइल गोर्बाचेव

Question ID : 2449922590

Status : Answered

Chosen Option :

Q.3 निम्नलिखित खिलाड़ियों में से किसने सबसे अधिक बार विंबलडन का महिला एकल खिताब जीता है?

Ans A. वीनस विलियम्स

B. मार्टिना नवरातिलोवा

C. सरेना विलियम्स

D. स्टेफी ग्राफ

Question ID : 2449922588

Status : Answered

Chosen Option :

Q.4

निम्नलिखित व्यक्तियों में से बांग्लादेश के पहले राष्ट्रपति कौन थे?

Ans A. परवेज मुशर्रफ

B. शेख हसीना

C. खालिदा जिया

D. शेख मुजीबुर रहमान

Question ID : 2449922583

Status : Answered

Chosen Option :

Q.5 In which city Humayun's tomb is located?

Ans A. New Delhi

B. Agra

C. Fatehpur Sikri

D. Sasaram

Question ID : 2449922586

Status : Answered

Chosen Option :

Q.6 श्री ई श्रीधरन निम्नलिखित में से किस संगठन के साथ सबसे घनिष्ठ रूप से जुड़े हुए हैं?

Ans A. भारतीय अंतरिक्ष अनुसंधान संगठन

B. नीति आयोग

C. कौकण रेलवे

D. भारतीय रिजर्व बैंक

Question ID : 2449922585

Status : Answered

Chosen Option :

Q.7 What is the capital of Hungary?

Ans A. Helsinki

B. Budapest

C. Lisbon

D. Brussels

Question ID : 2449922587

Status : Answered

Chosen Option :

Q.8 निम्नलिखित कथनों में से कौन-सा कथन सही है?

Ans A. सभी अक्षांश रेखायें उत्तरी एवं दक्षिणी ध्रुव पर मिलती हैं

B. भूमध्य रेखा कोलंबो से होकर गुजरती है

C. सभी देशान्तर रेखायें उत्तरी एवं दक्षिणी ध्रुव पर मिलती हैं

D. भूमध्य रेखा प्रयागराज (इलाहाबाद) से होकर गुजरती है

Question ID : 2449922582

Status : Answered

Chosen Option :

Q.9 Which scientist received the Bharat Ratna in the same year as Sachin Tendulkar?

Ans A. Anil Kakodkar

B. A.P.J. Abdul Kalam

C. C.N.R. Rao

D. V. Rajaraman

Question ID : 2449922581

Status : Answered

Chosen Option :

Q.1 Which of the following persons has not served as the Chief Minister of Uttar Pradesh?

Ans A. N. D. Tiwari

B. Govind Ballabh Pant

C. Sarojini Naidu

D. Chandra Bhanu Gupta

Question ID : 2449922589

Status : Answered

Chosen Option :

Section : Reasoning (1 Mark)

Q.1 Which one of the following pairs of vectors are orthogonal?

Ans A. $[1,2,4]^T$ and $[-3, 0, 1]^T$

B. $[1,2,4]^T$ and $[-2, -1, 1]^T$

C. $[1,2,4]^T$ and $[-12, -1, 1]^T$

D. $[1,2,4]^T$ and $[5, 0, -1]^T$

Question ID : 2449922592

Status : Answered

Chosen Option :

Q.2 $\lim_{t \rightarrow 0} \left(\frac{\sin t}{t} \right) =$

Ans A. undefined

B. 1

C. 0

D. -1

Question ID : 2449922591

Status : Answered

Chosen Option :

Q.3 मजदूरों के एक समूह ने 15 दिनों में काम करने का वादा किया था किन्तु उनमें से 5 मजदूर काम पर नहीं पहुंच पाये। यदि शेष मजदूरों का समूह 18 दिनों में इस काम को पूरा करता है, तो आरंभ में प्रस्तावित मजदूरों की संख्या ज्ञात करें।

Ans A. 25
 B. 30
 C. 35
 D. 20

Question ID : 2449922594

Status : Answered

Chosen Option :

Q.4 Which word does not belong with others?

Ans A. Tiger
 B. Lion
 C. Leopard
 D. Elephant

Question ID : 2449922593

Status : Answered

Chosen Option :

Q.5 Find the value of Z:

$$1=5$$

$$2=10$$

$$3=15$$

$$4=10$$

$$5=Z$$

Ans A. 1
 B. 0
 C. 20
 D. 25


Question ID : 2449922595

Status : Answered

Chosen Option :

Section : Reasoning (2 Mark)


Q.1

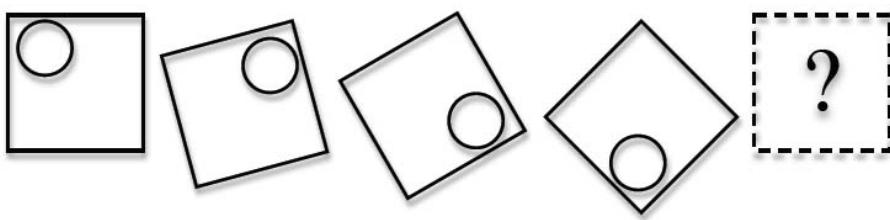


Which of the shapes below continues the sequence?

Ans


A.

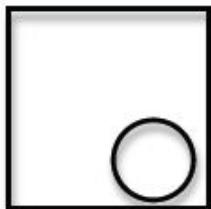


B.

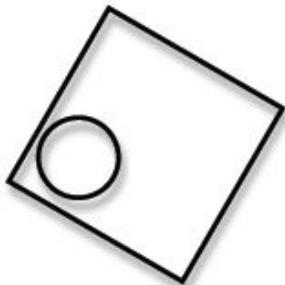

C.

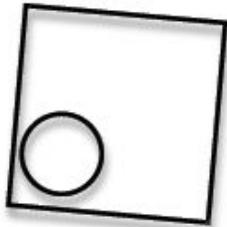

D.

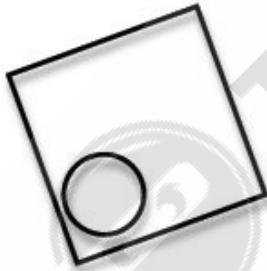

Question ID : 2449922598

Status : Answered

Chosen Option :

Q.2 Consider the matrix,

$$\mathbf{A} = \begin{bmatrix} a & b \\ 0 & c \end{bmatrix}$$

Eigenvalues of the matrix are given by

Ans A. $\lambda_1 = b, \lambda_2 = ac$

B. $\lambda_1 = a, \lambda_2 = c$

C. $\lambda_1 = 0, \lambda_2 = 0$

D. $\lambda_1 = ac, \lambda_2 = 0$

Question ID : 2449922597

Status : Answered

Chosen Option :

Q.3 Consider the following three systems of equations:

Case a: $x_1 + x_2 = 1, 2x_1 - x_2 = 0$

Case b: $x_1 + x_2 = 1, 2x_1 + 2x_2 = 2$

Case c: $x_1 + x_2 = 1, x_1 + x_2 = 0$

Which one of the following statements is true?

Ans A. None of the cases can be solved.

B.

Case a has many solutions; **case b** has unique solution; **case c** has no solution.

C.

Case a has no solution; **case b** has unique solution; **case c** has many solutions.

D.


Case a has unique solution; **case b** has many solutions; **case c** has no solution.

Question ID : 2449922596

Status : Answered



Chosen Option :

Q.4

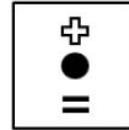


Which of the shapes below continues the sequence?

Ans

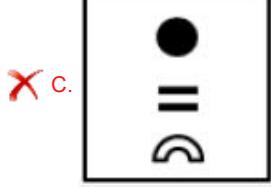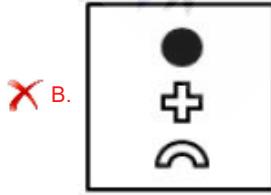

D.

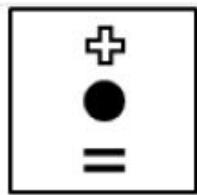

Question ID : 2449922599

Status : Answered

Chosen Option :

Q.5 Look at the series:

1, 1, 4, 9, 25, 64, __

What number should come next.

Ans

A. 144

B. 100

C. 169

D. 121

Question ID : 2449922600

Status : Answered

Chosen Option :

