



Teachingninja.in



Latest Govt Job updates



Private Job updates



Free Mock tests available

Visit - teachingninja.in



Teachingninja.in



SDSC (ISRO)

**Previous Year Paper
Technician B Electronic
Mechanic
4 June 2022**





भारत सरकार :: अंतरिक्ष विभाग
Government of India :: Dept. of Space

सतीश धवन अंतरिक्ष केंद्र शार, श्रीहरिकोटा

भारतीय अंतरिक्ष अनुसंधान संगठन
Indian Space Research Organisation



SATISH DHAWAN SPACE CENTRE SHAR Sriharikota

Participant ID	
Participant Name	
Test Center Name	
Test Date	04/06/2022
Test Time	4:30 PM - 6:30 PM
Subject	Electronic Mechanic(For SDSC SHAR and ISTRAC)

Section : Electronic Mechanic For SDSC SHAR and ISTRAC

Q.1 In electronics/electrical circuit the angle between voltage and current is called

- A. Peak factor
- B. Form factor
- C. Phase difference
- D. Power factor

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937644

Status : Answered

Chosen Option : D

Q.2 Convert the decimal number 292.75 to binary?

- A. 100100100.11
- B. 100010100.01
- C. 100100100.10
- D. 100011001.11

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937601

Status : Answered

Chosen Option : A

Q.3 Which of the following audio speaker will be hard to be driven by a power amplifier?

- A. 4 Ohms
- B. 8 Ohms
- C. 12 Ohms
- D. 2 Ohms

Ans A. A

B. B

C. C

D. D

Question ID : 5834937628

Status : **Answered**

Chosen Option : **C**

Q.4 The resolution of a 3½ digit, digital voltmeter assuming that the reference voltage is 2V is

- A. 0.5mV
- B. 2mV
- C. 6mV
- D. 1mV

Ans A. A

B. B

C. C

D. D

Question ID : 5834937637


Status : **Answered**

Chosen Option : **A**



Q.5

V_o in the following circuit is

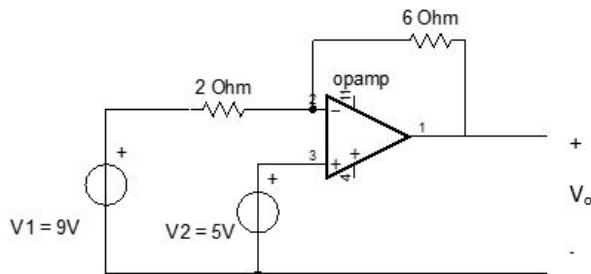

- A. 4V
- B. 17V
- C. 27V
- D. 12 V

Ans A. A

- B. B
- C. C
- D. D

Question ID : 5834937618

Status : Answered

Chosen Option : A

Q.6 The purpose of cold junction compensation for a thermocouple is

- A. To decrease the Temperature Sensitivity
- B. To increase voltage output
- C. To cancel unwanted voltage at the output of a Thermocouple
- D. Used for high temperature circuits

Ans A. A

- B. B
- C. C
- D. D

Question ID : 5834937638

Status : Answered

Chosen Option : C

Q.7 IP address size in IPV6 version is

- A. 216 bits
- B. 512 bits
- C. 32 bits
- D. 128 bits

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937629

Status : Answered

Chosen Option : B

Q.8 The SiO₂ layer in IC acts as

- A. a resistor
- B. an insulator
- C. an isolator
- D. channel

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937591

Status : Answered

Chosen Option : C

Q.9 A wire of resistance $3\ \Omega$ is cut into three equal pieces, which are then joined to form a triangle. The equivalent resistance between any two corners of the triangle is

- A. $2/3\ \Omega$
- B. $3/2\ \Omega$
- C. $1/2\ \Omega$
- D. $1/3\ \Omega$

Ans  A. A

 B. B
 C. C
 D. D

Question ID : 5834937661

Status : Answered

Chosen Option : D

Q.10 In voltage regulation Zener diode is used in

- A. Forward bias
- B. Reverse bias
- C. Cannot use Zener diode
- D. Forward bias with proper breakdown voltage

Ans  A. A
 B. B
 C. C
 D. D

Question ID : 5834937585

Status : Answered

Chosen Option : B



Q.11 Gain of an antenna is defined as the product of

- A. Antenna efficiency and directivity of the antenna
- B. Radiation intensity in that direction and the total input radiated power
- C. Radiation intensity in that direction and the average radiated power
- D. None of the above

Ans A. A

B. B

C. C

D. D

Question ID : 5834937625

Status : **Answered**

Chosen Option : **C**

Q.12 After firing an SCR, the gating pulse is removed, then the current in the SCR will

- A. Remains the same
- B. Immediately fall to zero
- C. Increase high
- D. Increase a little and fall to zero

Ans A. A

B. B

C. C

D. D

Question ID : 5834937647

Status : **Answered**

Chosen Option : **C**

Q.13 In a servo-controlled voltage stabilizer, what is the main method of operation?

- A. Open loop method
- B. Modulation method
- C. Closed loop method
- D. Voltage divider method

Ans A. A

B. B

C. C

D. D

Question ID : 5834937645

Status : **Answered**

Chosen Option : **D**

Q.14

Two conducting wires A (Resistance R_A) and B (Resistance R_B) are made of same material and have same length. If the diameter of the wire B is twice that of wire A, the ratio of R_A/R_B is?

- A. 4
- B. 1/4
- C. 1/2
- D. 1

Ans  A. A

-  B. B
-  C. C
-  D. D

Question ID : 5834937594

Status : **Answered**

Chosen Option : **C**

Q.15

The advantage of totem pole configuration is

- A. Fast and low power consumption
- B. Slow and high power consumption
- C. Fast and high power consumption
- D. None of the above

Ans  A. A

-  B. B
-  C. C
-  D. D

Question ID : 5834937588

Status : **Answered**

Chosen Option : **A**



Q.16 The phenomenon which causes the reverse breakdown in Zener Diode is called as

- A. Hall Effect
- B. Avalanche Effect
- C. Breakdown Effect
- D. Seebeck Effect

Ans A. A

B. B

C. C

D. D

Question ID : 5834937586

Status : **Answered**

Chosen Option : **B**

Q.17 The length of a tangent drawn from an external point, which is 10cm away from centre of circle is 8 cm. The radius of the circle is?

- A. 4 cm
- B. 5 cm
- C. 6 cm
- D. 7 cm

Ans A. A

B. B

C. C

D. D

Question ID : 5834937656

Status : **Answered**

Chosen Option : **B**

Q.18 In npn transistor, the majority carrier in the base region is

- A. Electrons
- B. Holes
- C. Atoms
- D. All

Ans A. A

B. B

C. C

D. D

Question ID : 5834937583

Status : **Answered**

Chosen Option : **A**

Q.19 In the frequency response curve of an RC coupled amplifier, drop in the gain value at lower frequencies observed is due to

- A. Output resistance of the input transistor
- B. Input resistance of the output transistor
- C. Reactance of coupling capacitor
- D. All of the above

Ans A. A

B. B

C. C

D. D

Question ID : 5834937650

Status : **Answered**

Chosen Option : D

Q.20 For a body moving with a constant speed in horizontal circle. Which of the following remain constant?

- A. Velocity
- B. Acceleration
- C. Centripetal force
- D. Kinetic energy

Ans A. A

B. B

C. C

D. D

Question ID : 5834937660

Status : **Answered**

Chosen Option : C



Q.21 A MOSFET in depletion mode acts as

- A. JFET
- B. a current Source
- C. a resistor
- D. a BJT

Ans ✓ A. A

✗ B. B

✗ C. C

✗ D. D

Question ID : 5834937587

Status : Answered

Chosen Option : B

Q.22 In Boolean logic if $XY=0$ then $X \oplus Y$ is equal to

- A. $X + Y$
- B. XY
- C. $\bar{X} \bar{Y}$
- D. $\bar{X} + \bar{Y}$

Ans ✓ A. A

✗ B. B

✗ C. C

✗ D. D

Question ID : 5834937603

Status : Answered

Chosen Option : D



Q.23 Which of the following method requires constant transmitter power for the signal transmission?

- A. Pulse Code Modulation
- B. Pulse Position Modulation
- C. Pulse Width Modulation
- D. Pulse Amplitude Modulation

Ans A. A

B. B

C. C

D. D

Question ID : 5834937633

Status : **Answered**

Chosen Option : **D**

Q.24 For a Non-inverting amplifier consisting of OPAMP, if A_{OL} and A_{CL} are Open loop and closed loop gains respectively, then

- A. $A_{OL} < A_{CL}$
- B. $A_{OL} = A_{CL}$
- C. $A_{OL} > A_{CL}$
- D. $A_{OL} < 1, A_{CL} < 1$

Ans A. A

B. B

C. C

D. D

Question ID : 5834937616

Status : **Answered**

Chosen Option : **B**

Q.25 What is the total impedance of RLC circuit, with resistance of 8Ω , capacitive reactance of 2Ω and inductive reactance of 8Ω connected in series across $230 \text{ V}, 50 \text{ Hz}$ supply?

- A. 12
- B. 18
- C. 14
- D. 10

Ans A. A

B. B

C. C


D. D

Question ID : 5834937614

Status : **Answered**

Chosen Option : **A**

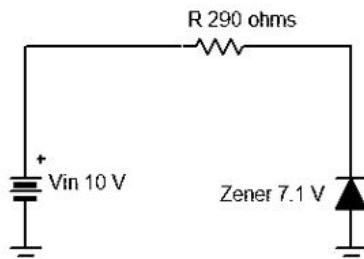Q.26 What is the current through the resistor in the circuit?



- A. 29 mA
- B. 2.9 mA
- C. 10 mA
- D. 12 mA


Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937589

Status : Answered

Chosen Option : A

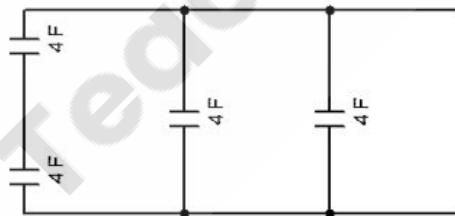Q.27 What is the total capacitance in the given circuit?



- A. 8 F
- B. 10 F
- C. 12 F
- D. 16 F

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937608

Status : Answered

Chosen Option : B

Q.28

A series resonant circuit has $L=1\text{ mH}$ and $C=10\text{ F}$. The required R for the bandwidth of 14 Hz is?

- A. $88\text{ m}\Omega$
- B. $0.14\text{ }\Omega$
- C. $159\text{ m}\Omega$
- D. $1.4\text{ }\Omega$

Ans  A. A

 B. B

 C. C

 D. D

Question ID : 5834937622

Status : Answered

Chosen Option : B

Q.29

The output of a logic gate is 1 when all its inputs are at logic 1. The gate is either

- A. NAND or NOR
- B. AND or OR
- C. OR or XOR
- D. AND or NOR

Ans  A. A

 B. B

 C. C

 D. D

Question ID : 5834937600

Status : Answered

Chosen Option : B



Q.30 The resistance value of PT100 sensor varies -----ohms/ $^{\circ}\text{C}$

- A. 0.184
- B. 0.284
- C. 0.384
- D. 0.484

Ans A. A

B. B

C. C

D. D

Question ID : 5834937636

Status : **Answered**

Chosen Option : **C**

Q.31 A 5V dc source is connected to a series combination of $100\ \Omega$ resistor and $0.2\ \mu\text{F}$ capacitor. What is the current through the circuit under steady state?

- A. 0.05 A
- B. 0.1 A
- C. 0.0 A
- D. 0.5 A

Ans A. A

B. B

C. C

D. D

Question ID : 5834937596

Status : **Answered**

Chosen Option : **A**



Q.32

Peak inverse voltage of a center tapped full wave rectifier is

- A. V_m
- B. $2 V_m$
- C. V_m / π
- D. $2 V_m / \pi$

Ans X A. A

- ✓ B. B
- X C. C
- X D. D

Question ID : 5834937643

Status : **Answered**

Chosen Option : B

Q.33 When we actuate a switch an output lamp will be ON, and when we de-actuate the same switch the output Lamp still glows ON. What kind of circuit it is?

- A. Open Circuit
- B. Inching Circuit
- C. Latching Circuit
- D. Interlocking Circuit

Ans X A. A

- X B. B
- ✓ C. C
- X D. D

Question ID : 5834937635

Status : **Answered**

Chosen Option : D



Q.34 Which of the following is not a type of Strain Gauge?

- A. Wire
- B. Foil
- C. Frame
- D. Coil


Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937640

Status : **Answered**

Chosen Option : C

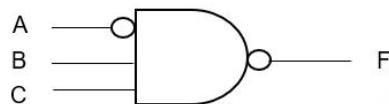Q.35 What is the input of the below given gates in the form of ABC, if the output F=0?



- A. 001
- B. 110
- C. 011
- D. 100

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937606

Status : **Answered**

Chosen Option : C



Q.36 Which of the following is not a basic reason for modulation of signal?

- A. Practical length of antenna
- B. Operating range
- C. Wireless communication
- D. Encode an information

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937627

Status : Answered

Chosen Option : A

Q.37 In an inverter, if the fundamental output frequency is 50Hz, then the frequency of the lowest order harmonic will be

- A. 50 Hz
- B. 150Hz
- C. 250Hz
- D. 350Hz

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937652

Status : Answered

Chosen Option : A

Q.38 For a 256B ROM which is represented as 512 X 4 bits. The size of address and data lines respectively are

- A. 512 and 4 bits
- B. 9 and 4 bits
- C. 9 and 2 bits
- D. 512 and 2 bits

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937604

Status : Answered

Chosen Option : D

Q.39 In Common Base configuration of transistor $\alpha = 0.9$ and $I_E = 1\text{mA}$, find I_B

- A. 1 A
- B. 10 mA
- C. 5 mA
- D. 0.1 mA

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937621

Status : **Answered**

Chosen Option : **D**

Q.40 The sum of three numbers is 264. If first number is twice the second and third number is one-third of the first, then the second number is

- A. 48
- B. 54
- C. 72
- D. 84

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937654

Status : **Answered**

Chosen Option : **B**



Q.41 In full adder, there are

- A. Two binary inputs and two outputs
- B. Three binary inputs and two binary outputs
- C. Three binary inputs and three binary outputs
- D. Two binary inputs and three Binary outputs

Ans A. A

B. B

C. C


D. D

Question ID : 5834937602

Status : Answered

Chosen Option : A

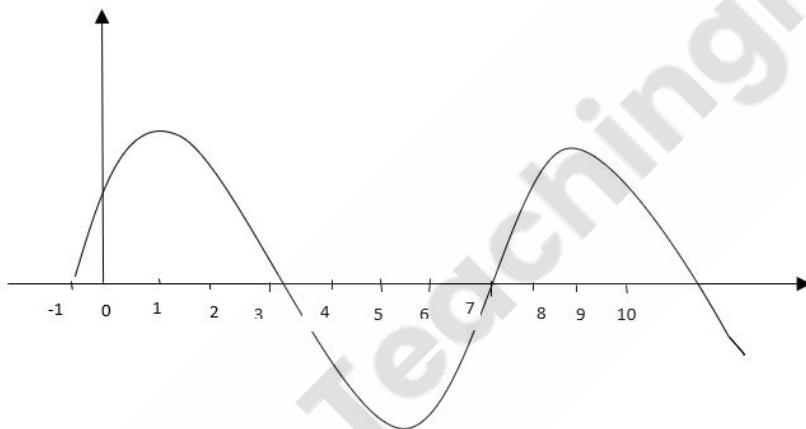Q.42 What is the period and frequency of the waveform shown below?



- A. $T = 10\text{sec}$ and $F = 0.100\text{Hz}$
- B. $T = 5\text{sec}$ and $F = 0.200\text{Hz}$
- C. $T = 7\text{sec}$ and $F = 0.100\text{Hz}$
- D. $T = 8\text{sec}$ and $F = 0.125\text{Hz}$

Ans A. A

B. B

C. C

D. D

Question ID : 5834937623

Status : Answered

Chosen Option : C

Q.43 Which splicing technique involves the alignment and locking of broken fiber edges by means of positioning devices and optical cement?

- A. Fusion
- B. Mechanical
- C. Both A and B
- D. None of the above

Ans A. A


- B. B
- C. C
- D. D

Question ID : 5834937631

Status : **Answered**

Chosen Option : A

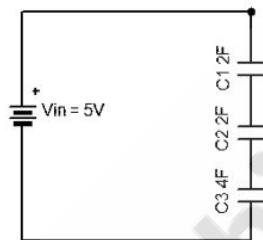Q.44 What is the voltage across C1, C2 and C3 respectively in the given circuit if they are fully charged?



- A. 2 V, 2 V, 1 V
- B. 1.5 V, 1.5 V, 2 V
- C. 1 V, 1 V, 3 V
- D. 3 V, 1 V, 1 V

Ans A. A

- B. B
- C. C
- D. D

Question ID : 5834937595


Status : **Answered**

Chosen Option : A

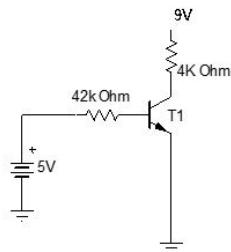Q.45

What is the state of following transistor in the circuit? $h_{FE}(\beta) = 100$,

$$V_{BE} = 0.8 \text{ V}, V_{CE \text{ sat}} = 0.2 \text{ V}$$



- A. Active region
- B. Saturated region
- C. Cutoff region
- D. Cannot be determined

Ans X A. A

- ✓ B. B
- X C. C
- X D. D

Question ID : 5834937593

Status : Answered

Chosen Option : B

Q.46 Which of the following oscillator cannot be used in low frequency applications

- A. Wein Bridge oscillators
- B. RC phase shift oscillators
- C. Colpitts oscillators
- D. Blocking oscillators

Ans X A. A

- X B. B
- ✓ C. C
- X D. D

Question ID : 5834937617

Status : Answered

Chosen Option : D

Q.47 The Peak inverse voltage of each diode in bridge rectifier circuit is ____ that of the equivalent center tapped full wave rectifier circuit.

- A. Half
- B. The same
- C. Twice
- D. Four times

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937641

Status : **Answered**

Chosen Option : A

Q.48 What is device show below?



- A. N-MOS
- B. P-MOS
- C. CMOS
- D. JFET

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937592

Status : **Answered**

Chosen Option : B

Q.49 The maximum rate of change of output voltage caused by a step input voltage of an OPAMP is called

- A. Slew rate
- B. Nyquist rate
- C. Distortion rate
- D. Rising rate

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937612

Status : **Answered**

Chosen Option : A

Q.50 Maximum component density for a given PCB size can be obtained by

- A. SMD components and multi-layer PCB
- B. Leaded components and single sided PCB
- C. Leaded components and double-sided PCB
- D. SMD components and double-sided PCB

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937609

Status : **Answered**

Chosen Option : D

Q.51 Logic equation of an EX-NOR gate having its inputs as A and B is?

- A. $A'B + AB'$
- B. $A'B' + A'B$
- C. $A'B' + AB$
- D. $A'B' + AB'$

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937630

Status : **Answered**

Chosen Option : D

Q.52

A transistor has a β_{dc} of 120 and base current of 10 μ A. what is the collector current?

- A. 1.2 mA
- B. 120 μ A
- C. 12 mA
- D. 120 mA

Ans  A. A

 B. B
 C. C
 D. D

Question ID : 5834937615

Status : **Answered**

Chosen Option : D

Q.53 Pulsating DC applied to power amplifier causes

- A. Burning of transistor
- B. Hum in the circuit
- C. Excessive forward voltage
- D. Nothing happens

Ans  A. A
 B. B
 C. C
 D. D

Question ID : 5834937649

Status : **Answered**

Chosen Option : B

Q.54

Which of the following is correct for a D-type flip flop?

- A. The output toggles if one of the inputs is held '1'
- B. Only one of the inputs can be '1' at a time
- C. The output complement follows the input when enabled
- D. The Q output is either 'Set' or 'Reset' as soon as the D input goes '1' or '0'

Ans  A. A
 B. B
 C. C
 D. D

Question ID : 5834937607

Status : **Answered**

Chosen Option : D

Q.55 Find the square root of $(272^2 - 128^2)$

- A. 144
- B. 200
- C. 240
- D. 256

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937655

Status : Answered

Chosen Option : D

Q.56 The advantage of FDMA over TDMA includes

1. Division is simpler
2. Propagation delays are eliminated
3. Cheaper filters with less complicated logic functions
4. Linearity

- A. 1,2 and 3 correct
- B. 1 and 2 are correct
- C. 1 and 4 correct
- D. All four are correct

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937632

Status : Answered

Chosen Option : D

Q.57 Which gauge is used for measurement of Vacuum pressure?

- A. McLeod gauge
- B. Bellows gauge
- C. Both A & B
- D. None of the above

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937642

Status : Answered

Chosen Option : C

Q.58 What is the logic levels 0 and 1 respectively for RS232 serial communication standard?

- A. +5 to +15V and -5 to -15V
- B. +2 to +6V and -2 to -6V
- C. +3 to +12V and -3 to -12V
- D. +2 to +16V and -2 to -16V

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937626

Status : Answered

Chosen Option : D

Q.59 If $\sqrt{2} \sin(60 - \alpha) = 1$ then α is

- A. 45°
- B. 15°
- C. 60°
- D. 30°

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937653

Status : Answered

Chosen Option : A

Q.60 A 1000 J work is done in 2 seconds. What is the power utilized?

- A. 998 W
- B. 1002 W
- C. 2000 W
- D. 500 W

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937658

Status : Answered

Chosen Option : A

Q.61 A body of mass 10 kg is travelling with uniform speed of 5 m/s. Its kinetic energy is

- A. 25 J
- B. 125 J
- C. 1250 J
- D. 1000 J

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937659

Status : Answered

Chosen Option : B

Q.62 A decade counter is a combination of

- A. Four shift registers
- B. Four flip flops
- C. Four flip flops and combinational circuit
- D. Three flipflops.


Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937605

Status : Answered

Chosen Option : C

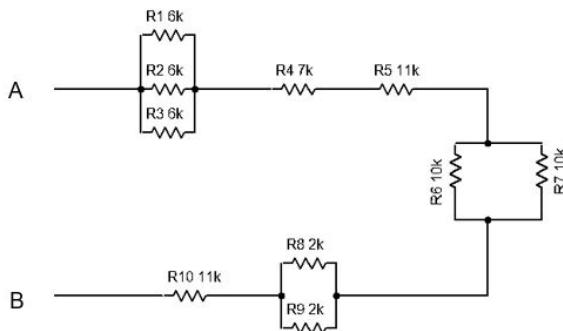Q.63 Find the resistance between the points A and B in the circuit given below? The resistance values given the circuit are kilo Ohms (i.e. 2k means $2\text{k}\Omega$).



- A. $35\text{k}\Omega$
- B. $38\text{k}\Omega$
- C. $47\text{k}\Omega$
- D. $37\text{k}\Omega$

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937611
Status : Answered
Chosen Option : D

Q.64 Which one of the following is not an essential component in a Clamper Circuit?


- A. Diode
- B. Capacitor
- C. Resistor
- D. Independent DC Supply

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937610
Status : Answered
Chosen Option : B

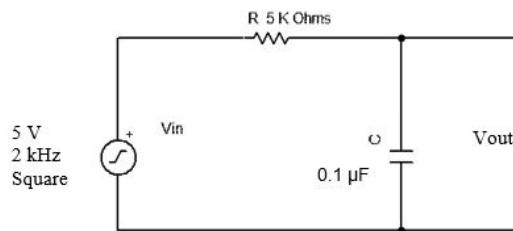Q.65

A 1 kHz square wave is applied to the circuit below. The output waveform will look like



- A. Sine
- B. Triangular
- C. Sawtooth
- D. Square

Ans A. A

B. B

C. C

D. D

Question ID : 5834937620

Status : Answered

Chosen Option : A

Q.66

The quality factor 'Q' of an inductance coil is improved by?

- A. Reducing coil resistance to minimum
- B. Reducing coil inductance
- C. Increasing the coil resistance to the maximum
- D. Both (A) and (B)

Ans A. A

B. B

C. C

D. D

Question ID : 5834937648

Status : Answered

Chosen Option : D

Q.67 A sphere and a cube have equal surface areas. The ratio of the volume of the sphere to that of cube is

- A. $\sqrt{\pi} : \sqrt{6}$
- B. $\sqrt{6} : \sqrt{\pi}$
- C. $\sqrt{\pi} : \sqrt{3}$
- D. $\sqrt{3} : \sqrt{\pi}$

Ans A. A

- B. B
- C. C
- D. D

Question ID : 5834937657

Status : Answered

Chosen Option : A

Q.68 Which of transistor configurations has high voltage gain and high current gain?

- A. CC
- B. CB
- C. CE
- D. Both CB and CC

Ans A. A

- B. B
- C. C
- D. D

Question ID : 5834937590

Status : Answered

Chosen Option : D

Q.69 If any input of TTL circuit is left floating it functions as if it is connected to

- A. 0 level
- B. High impedance level
- C. 1 level
- D. Don't care

Ans A. A

- B. B
- C. C
- D. D

Question ID : 5834937598

Status : Answered

Chosen Option : B

Q.70 What is DDR -DRAM ?

- A. Dynamic Data Rate Double Random Access Memory
- B. Double Data Rate Dynamic Random Access Memory
- C. Dynamic Data Register Double Random Access Memory
- D. Digital Data Register Dynamic Random Access Memory

Ans A. A
 B. B
 C. C
 D. D


Question ID : 5834937599

Status : **Answered**

Chosen Option : **D**

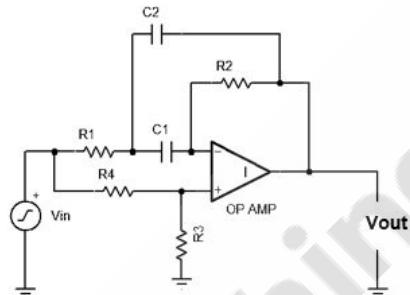Q.71

What is the functionality of the given circuit below?



- A. Band Pass Filter
- B. Low Pass Filter
- C. Band Stop Filter
- D. High Pass Filter

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937619

Status : **Answered**

Chosen Option : **A**

Q.72 The frequencies allotted for FM broadcasting is

- A. 88MHz - 108MHz
- B. 10MHz - 30MHz
- C. 50MHz - 170MHz
- D. 60MHz - 80MHz

Ans ✓ A. A
✗ B. B
✗ C. C
✗ D. D

Question ID : 5834937624
Status : Answered
Chosen Option : A

Q.73 In a CRO, what is the calibration signal generally available?

- A. DC
- B. Sawtooth
- C. Sine
- D. Square

Ans ✗ A. A
✓ B. B
✗ C. C
✗ D. D

Question ID : 5834937634
Status : Answered
Chosen Option : C

Q.74 What is the output waveform of a comparator circuit, if the input is Sine wave?

- A. Rectangular wave
- B. Sinewave
- C. Ramp wave
- D. Sawtooth wave

Ans A. A

B. B
 C. C
 D. D

Question ID : 5834937639
Status : Answered
Chosen Option : C

Q.75 The difference between Latch and Flip flop is

- A. Latch is edge triggered, Flip flop is level triggered
- B. Latch is level triggered, Flip flop is edge triggered
- C. Both are level triggered
- D. Both are edge triggered

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937597
Status : Answered
Chosen Option : A

Q.76 At room temperature, an intrinsic silicon crystal acts as

- A. a battery
- B. a conductor
- C. an insulator
- D. a capacitor

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937584
Status : Answered
Chosen Option : C

Q.77 If a transformer has turn ratio of 1:2 and the primary current is 20A then, what will be the secondary current?

- A. 40A
- B. 20A
- C. 10A
- D. 100A


Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937646

Status : Answered

Chosen Option : A

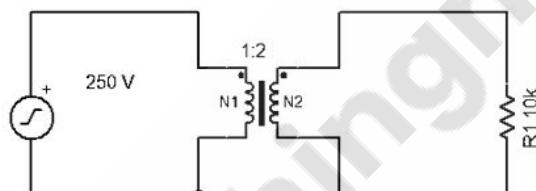Q.78 If the transformer given is ideal transformer, then what is the power dissipated in the primary of the transformer given?



- A. 250 W
- B. 0.25 W
- C. 50 W
- D. 25 W

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937651

Status : Answered

Chosen Option : C

Q.79 Which of the following conditions are needed to properly bias a NPN transistor amplifier?

- A. Forward bias the base-emitter junction and reverse bias the base collector junction.
- B. Forward bias the collector-base junction and reverse bias the emitter-base junction
- C. Apply a positive voltage on the n-type material and a negative voltage on the p-type material
- D. Apply a large voltage on the base


Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937582

Status : **Answered**

Chosen Option : A

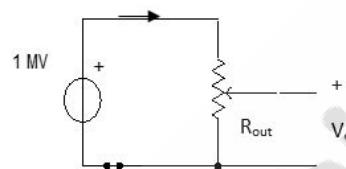Q.80 What is the value of R_{out} for the voltage divider circuit given below so that current I is limited to 0.5A when V_o is 100V?



- A. $2M\Omega$
- B. $2k\Omega$
- C. 200Ω
- D. 2Ω

Ans A. A
 B. B
 C. C
 D. D

Question ID : 5834937613

Status : **Answered**

Chosen Option : B